

## **Lab 6 Grading Standard:**

- 1) *In grading, do not explicitly assign points to the various sections. Rather, take points off for incorrect, incomplete or missing items.*
- 2) *When you take point off, be sure to write a short comment as to why the points were lost.*
- 3) *Example: (-1) What is the measured value of the component?  
(-3) What is the mathematical formula that you are plotting on top of your data?*

### **General Notes:**

- The axis of all plots must be labeled. This should include the quantity, the units and numerical values.
- The boxed questions should be answered in the lab book.
- Procedures must have a circuit diagram.
- Measured values of components used should be recorded in the lab book.
- Relevant formulas should be included in the lab book.
- Formulas for computed quantities in tables should be near the table in the book.

Failure to measure a component value when possible (max -1 per occurrence)

Missing units on components, plot axes, tables ... (-1 per occurrence).

Missing plot (-4 per occurrence).

Missing axes labels on plots (-1 per label).

Missing column labels on tables (-1 per label).

Missing formula for computed quantity in table (-1 per table)--can be in column title

Missing important formulas (-2 per occurrence)

No fit to linear curves (-2 per occurrence).

No fit values with units (-2 per occurrence).

No comparison of fit values with expectations when possible (-2 per occurrence).

Missing theoretical calculations, including formulas (-3 per occurrence).

Failure to answer questions (-2 per question, maximum of -10)

**Pre-lab Signature:** 10

**Purpose/Introduction** 5

There should be a two to five line description of what they are going to do in this lab. This is all or nothing for five points.

### **The IV curve of the 1N4004 Diode:**

Procedure: 5

There should be a several line procedure that shows the circuit, indicates where they are going to measure voltages, what the measured values of the components are.

Data: 5

The data need to be plotted on an IV curve

Analysis: 10

Fit the diode IV curve to the Shockley equation to obtain  $m$  and  $I_s$ .

### **The Clamp Circuit:**

Procedure: 5

The procedure should include circuit diagrams, measured values of components and a description of what they are going to do.

Data: 10

There should be an IV curve for the data.

Analysis: 10

An estimate should be provided for both the diode voltage drop,  $V_d$  and the output resistance of the clamp circuit. Include the relevant formulas.

### **The Voltage Doubler:**

Procedure 5

Data: 10

Measure both the IV curve at 1kHz and the frequency dependence for a 220k-Ohm load.

Analysis: What is the output impedance of the doubler? Include the relevant formulas.

### **The Voltage Multiplier:**

Procedure: 5

Data: 10

Produce IV curves for the three frequencies.

Analysis: 10

What are the output impedances for the three frequencies? These do not agree with the expected values, probably because the diode-drop voltage changes in an unclear way. The fact that something funny is going on is obvious by the curved shape of the IV curve. Include the relevant formulas.

**Questions** 10

**Conclusion/Summary** 5